

OBSERVATION:-

INPUT CHARACTERISTICS OF COMMON EMITTER TRANSISTOR:-

S.No	$V_{CE} = 2V$		$V_{CE} = 4V$	
	$V_{BE} (V)$	$I_B (\mu A)$	$V_{BE} (V)$	$I_B (\mu A)$
1	0 to 0.69	0	0 to 0.72	0
2	0.73	1	0.75	1
3	0.75	3	0.764	3
4	0.77	5	0.78	5
5	0.78	7	0.79	7
6	0.80	10	0.81	10

OUTPUT CHARACTERISTICS OF COMMON EMITTER TRANSISTOR:-

S.No	$I_B = 80 \mu A$		$I_B = 100 \mu A$	
	$V_{CE} (V)$	$I_C (mA)$	$V_{CE} (V)$	$I_C (mA)$
1	1	1	1	2
2	2	3	2	4
3	3	5	3	6
4	4	5	4	7
5	5	5	5	7
6	6	5	6	7
7	7	5	7	7

PROCEDURE:-

INPUT CHARACTERISTICS OF CE TRANSISTOR:-

- Connect the circuit as per the circuit diagram.
- For plotting the input characteristics, the output voltage V_{CE} is kept constant at $2V$ and for different values of V_{BE} . Note down the values of I_B .
- Repeat the above step by keeping V_{CE} at $4V$.
- Tabulate all the readings.
- Plot the graph between V_{BE} and I_B for constant V_{CE} .


OUTPUT CHARACTERISTICS OF CE TRANSISTOR:-

- Connect the circuit as per the circuit diagram.
- For plotting the output characteristics, the input current I_B is kept constant at $80 \mu A$ and for different values of V_{CE} note down the values of I_C .
- Repeat the above step by keeping I_B at $100 \mu A$.
- Tabulate the readings.
- Plot the graph between V_{CE} and I_C for constant I_B .


RESULT:-

Thus, the input and output characteristics of a transistor in CE configuration are drawn.


MOSFET CHARACTERISTICS CIRCUIT DIAGRAM:-

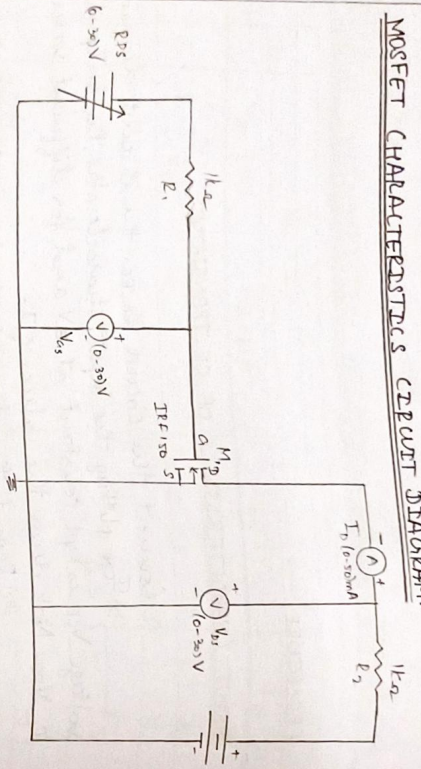

MODEL GRAPH:- TRANSFER CHARACTERISTICS:-

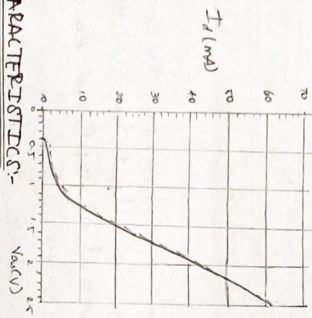

DRAIN CHARACTERISTICS:-

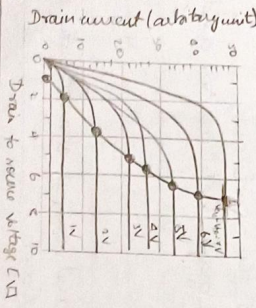

Ex:- OF
Date:- 15/9/23

CHARACTERISTICS OF METAL OXIDE SEMICONDUCTOR FIELD EFFECT TRANSISTOR (MOSFET)

AIM:-

To obtain the drain characteristics and transfer characteristics of MOSFET.

APPARATUS REQUIRED:-

S.No	APPARATUS	TYPE	RANGE	QUANTITY
1	MOSFET	150		1
2	Resistor		500Ω, 1kΩ	1 each
3	DC power supply		5V	1 each
4	Connecting wires			

OBSERVATION:-

DRAIN CHARACTERISTICS		TRANSFER CHARACTERISTICS	
$V_{DS} = 4.5V$		$V_{DS} = 4.5V$	
V_{GS}	I_D	V_{GS}	I_D
0	0	0	0
0.5	0.5	0.5	0
1	1	4	0
1.5	1.2	4.2	1
2	1.9	4.4	2
2.5	2.2	4.6	3.8
3	2.8	5	4
3.5	3.1		
4	3.5		
4.5	4		
5	4.1		
5.5	4.2		
6	4.2		

PROCEDURE:-

TRANSFER CHARACTERISTICS:-

- Draw the MOSFET as per the circuit diagram.
- Keep the $V_{DS} = 10V$ and $V_{GS} = 4.5V$
- Set the DC sweep primary and secondary values.
- Place the voltage probe at source of MOSFET and verify the circuit.

DRAIN CHARACTERISTICS:-

- Draw the MOSFET as per the circuit diagram.
- Keep the $V_{GS} = 4.5V$ and $V_{DS} = 10V$
- Set the DC sweep primary and secondary values.
- Place the voltage probe at source of MOSFET and verify the circuit.

RESULT:-

The drain characteristics and Transfer characteristics of MOSFET was verified.

21/11/23