



SRM INSTITUTE OF SCIENCE AND TECHNOLOGY

TIRUCHIRAPPALLI CAMPUS

NAME : E. G. PRADEEP

SUB : DIGITAL LOGIC DESIGN

DEPARTMENT : B.TECH. ECE

ASSIGNMENT - II



1. A, B, B_{in}, D and B_{out} are respectively the minuend, the subtrahend, the BORROW-IN, the difference output and the BORROW-OUT in the case of a full subtractor. Determine the bpt status of D and B_{out} for the following values of A, B and B_{in}

(a) $A=0, B=1, B_{in}=1$ (b) $A=1, B=1, B_{in}=0$


(c) $A=1, B=1, B_{in}=1$ (d) $A=0, B=0, B_{in}=1$

Ans: Design of full subtractor

(i) Problem statement:

FULL subtractor

ii) Block diagram

 



iii) Truth table

A	B	B_{in}	\oplus	B_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

iv) IC-MAP

For Difference

B_{in}	00	01	11	10
A				
0	0	1	3	2
1	4	5	7	6

$$\oplus = AB'B_{in} + A'B'B_{in} +$$

$$ABB_{in} + A'B B_{in}$$

For Borrow

B	B_{in}				
A					
0	1	2	3	4	5
1	6	7	8	9	10

$$B_{out} = A'B_{in} + A'B +$$

$$B B_{in}$$

$$= B_{in}(A+B) + A'B$$



(a) $A = 0, B = 1, B_{in} = 1 \Rightarrow D = 0 ; B_{out} = 1$

(b) $A = 1, B = 1, B_{in} = 0 \Rightarrow D = 0 ; B_{out} = 0$

(c) $A = 1, B = 1, B_{in} = 1 \Rightarrow D = 1 ; B_{out} = 1$

(d) $A = 0, B = 0, B_{in} = 1 \Rightarrow D = 1 ; B_{out} = 1$

2. Determine the number of half and full adder circuits blocks required to construct a 64-bit binary parallel adder. Also, determine the number and type of additional logic gates needed to transform this 64-bit adder into a 64-bit adder-subtractor.

Ans:

For 64 bit:

Half adder = 1 ; Full adder = 63

For 64 bit adder-subtractor-

No. of additional logic gates = $64 + 64 = 128$ gates


Types of additional logic gates = XOR & AND gate



* From the above logic diagram. It is seen that Y (DIFFERENCE) is $A \oplus B$ that is EX-OR and X (BORROW) is $A'B$ (AND GATE).


4. Implement the Boolean function with a suitable multiplexer $f(A, B, C) = \pi(1, 2, 5)$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 


 
$$\begin{aligned} Y &= A'B'C' + A'BC' + AB'C + ABC' + ABC \\ &= A'C'(B' + B) + AB(C' + C) + AB'C \\ &= A'C' + AB + AB'C \\ &= A'C' + A(B + B' + C) \\ &= A'C' + A(B + C) \\ &= A'C' + AB + AC \\ &= (A \oplus C) + AB \end{aligned}$$





6. A combinational circuit is defined by $F = \Sigma(0, 2, 5, 6, 7)$. Hardware implement the Boolean functions F with a suitable decoder and an external OR/NOR gate having the minimum number of inputs.

Ans:

A	B	C	Y Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1