




SRM INSTITUTE OF SCIENCE AND TECHNOLOGY

TIRUCHIRAPPALLI CAMPUS

Q1. A, B, Bin, D and Bout are respectively the minuend, the subtrahend, the BORROW-IN, the DIFFERENCE output and the Borrow out in the case of full subtractor. Determine the bit status of D and Bout for the following values of A, B and Bin

Block diagram:

 

Truth table for full subtractor

Deci	A	B	Bin	D	Bout
0	0	0	0	0	0
1	0	0	1	1	1
2	0	1	0	1	1
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	0
6	1	1	0	0	0
7	1	1	1	1	1

K-MAP

i) Difference

	Bin B'Bin'	B'Bin	BBin	BBin'
A		1		1
A'	0	1	3	2
A	1	4	5	6

$$D = AB'B'in + A'B'Bin + ABBin + ABBin'$$

ii) Borrow out

	Bin B'Bin'	B'Bin	BBin	BBin'
A		1		1
A'	0	1	3	2
A	1	4	5	6

$$Bout = A'Bin + A'B + ABBin$$

$$Bout = A'B + Bin(A'+B)$$



a) $A = 0$; $B = 1$; $B_{in} = 1$

$$D = 0 ; B_{out} = 1$$

b) $A = 1$; $B = 1$; $B_{in} = 0$

$$D = 0 ; B_{out} = 0$$

c) $A = 1$; $B = 1$; $B_{in} = 1$

$$D = 1 ; B_{out} = 1$$

d) $A = 0$; $B = 0$; $B_{in} = 1$

$$D = 1 ; B_{out} = 1$$

2) Determine the number of half and full adder circuit blocks required to construct a 64 bit binary parallel adder. Also, determine the number and type of additional logic gates needed to transform this 64 bit adder subtractor

i) An 64 bit binary parallel adder requires 1 half adder and 63 full adder

ii) To transform a 64 bit adder into a 64 bit adder subtractor we need to add 64 XOR gate and 64 AND gate.

$$\bullet \text{ XOR and AND gate} = 64$$

$$\bullet \text{ Total no. of logical gate} = 128$$


$$[64 \text{ bit adder}] + [64 \text{ XOR gate}] + [64 \text{ AND gate}] = 64 \text{ bit adder subtractor}$$



SRM INSTITUTE OF SCIENCE AND TECHNOLOGY

TIRUCHIRAPPALLI CAMPUS

 3) Prove that the logic diagram from the figure performs the function of a half-subtractor provided that Y represents the DIFFERENCE output and X- represent the BORROW output



TRUTH TABLE.

A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

K-MAP

A) DIFFERENCE

A \ B	B'	B
A'	0	1
A	1	0

$$Y = A'B + AB'$$

$$Y = A \oplus B$$

B) BORROW

A \ B	B'	B
A'	0	1
A	0	0

$$X = A'B$$

For Borrow $\rightarrow A'B$
For Difference $\rightarrow A \oplus B$

From the above logic diagram, it is clear that $y = A \oplus B$ which is EX-OR and x is $A'B$ (AND gate).

hence it is proved.




SRM INSTITUTE OF SCIENCE AND TECHNOLOGY

TIRUCHIRAPPALLI CAMPUS

4) Implement the Boolean function with a suitable multiplexer

$$y(A, B, C) = \pi(1, 2, 3)$$

D	A	B	C	y
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

 


4x1 Multiplexer



SRM INSTITUTE OF SCIENCE AND TECHNOLOGY
TIRUCHIRAPPALLI CAMPUS

Q5. Design a 10 line decimal to BCD priority encoder:

D	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	D ₈	D ₉	A	B	C	D
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	x	1	0	0	0	0	0	0	0	0	0	0	0	1
2	x	x	1	0	0	0	0	0	0	0	0	0	1	0
3	x	x	x	1	0	0	0	0	0	0	0	0	1	1
4	x	x	x	x	1	0	0	0	0	0	0	1	0	0
5	x	x	x	x	x	1	0	0	0	0	0	1	0	1
6	x	x	x	x	x	x	1	0	0	0	0	1	1	0
7	x	x	x	x	x	x	x	1	0	0	0	1	1	1
8	x	x	x	x	x	x	x	x	1	0	1	0	0	0
9	x	x	x	x	x	x	x	x	x	1	1	0	0	1

 



SRM INSTITUTE OF SCIENCE AND TECHNOLOGY
TIRUCHIRAPPALLI CAMPUS

6) A combinational circuit is defined by $F = \sum (0, 2, 5, 6, 7)$
Hardware implement the Boolean function F with a suitable decoder and an external OR/NOR gate having the minimum number of inputs

D	A	B	C	Y
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

$$Y = A'B'C' + A'BC' + AB'C' + ABC' + ABC$$

$$Y = A'C'(B' + B) + AB(C' + C) + ABC$$

$$Y = A'C' + AB + ABC$$

$$Y = A'C' + A(B + B'C)$$

$$Y = A'B'C' + A'(BC' + B'C) + ABC' + ABC$$

$$Y = A'(BC' + B'C) + ABC'$$

$$Y = A'(B \oplus C) + ABC'$$

$$Y = (A \oplus C)' + AB$$

